

# Problem Set 3

---

Justin Ely

605.411 Foundations of Computer Architecture

20 September, 2016

---

1)

For this, and following solutions, (n) represents column n in the table. This is used to reduce errors in typing when doing arithmetic with derived columns.

1	2	3	4	5	6	7
a	b	$(ab)'$	$A'(3)$	$B'(3)$	$((4)(5))'$	$((6)(6))'$
0	0	1	1	1	0	1
1	0	1	0	1	1	0
0	1	1	1	0	1	0
1	1	0	1	1	0	1

The result (column 7) has the same truth table as a XNOR gate.

2)

ROW	A	B	C	Y	Maxterm	Minterm
0	0	0	0	1		$A'B'C'$
1	0	0	1	0	$A + B + C'$	
2	0	1	0	1		$A'BC'$
3	0	1	1	1		$A'BC$
4	1	0	0	0	$A' + B + C$	
5	1	0	1	0	$A' + B + C'$	
6	1	1	0	1		$ABC'$
7	1	1	1	0	$A' + B' + C'$	

**3a)**

1	2	3	4	5	6	7
a	b	c	ab	bc	ac	(4) + (5) + (6)
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	0	0
1	0	1	0	0	1	1
1	1	0	1	0	0	1
1	1	1	1	1	1	1

**3b)**

$AB + BC + AC$

**4)**

1	2	3	4	5	6
a	b	ab	a'b'	(3) + (4)	(5)'
0	0	0	1	1	0
1	0	0	0	0	1
0	1	0	0	0	1
1	1	1	0	1	0

This logic circuit can be replaced with a single XOR gate.

**5)**

From the circuit diagram shown:

$$1. o_3 = S'I_2$$

$$2. o_2 = SI_3 + S'I_1$$

$$3. o_1 = I_2S + S'I_0$$


$$4. o_0 = I_1S$$

Thus, by setting  $S = 1$ , and  $I_3, I_2, I_1, I_0 = 1011$ , the circuit comes out as:  
 $o_3, o_2, o_1, o_0 = 0101$ .

6)

From problem 1, column 6 is the same output as an XOR gate, and has been constructed with only NAND gates. Thus, the circuit would look like that shown in the figure below.

Figure 1: Circuit diagram for an XOR gate using only NAND gates.

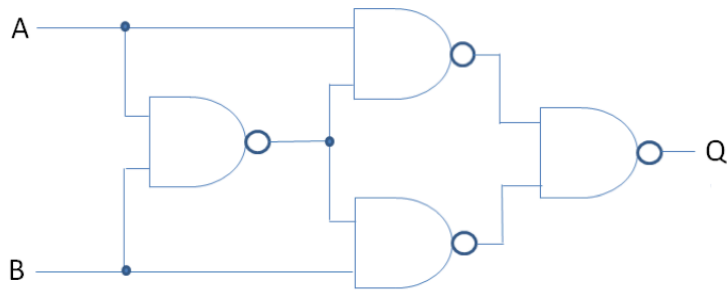

7)

1	2	3	4	5	6	7	8	9
A	B	$A'B$	$AB'$	$A'B + AB'$	C	$(5)'C$	$C'(5)$	R
0	0	0	0	0	0	0	0	0
0	0	0	0	0	1	1	0	1
0	1	1	0	1	0	0	1	1
0	1	1	0	1	1	0	0	0
1	0	0	1	1	0	0	1	1
1	0	0	1	1	1	0	0	0
1	1	0	0	0	0	0	0	0
1	1	0	0	0	1	1	0	1

8a)

A	B	C	Z	Minterm
0	0	0	1	$A'B'C'$
0	0	1	0	$A'B'C$
0	1	0	0	$A'BC'$
0	1	1	1	$A'BC$
1	0	0	1	$AB'C'$
1	0	1	0	$AB'C$
1	1	0	0	$ABC'$
1	1	1	1	$ABC$

The function Z is then built of the minterms on rows where Z=1:  $Z = A'B'C' + A'BC + AB'C' + ABC$ .

8b)

$$Z = A'B'C' + A'BC + AB'C' + ABC \quad (1)$$

$$Z = B'C'(A' + A) + BC(A' + A) \quad (2)$$

$$Z = B'C' + BC \quad (3)$$

## Appendix

Jupyter notebook with python code showing verification of problems is attached:

# hw3

September 20, 2016

## 0.1 Utility functions to facilitate computations

```
In [48]: def nand(a, b):  
         return not a & b
```

```
In [49]: def _and(a, b):  
         return a & b
```

```
In [50]: def _or(a, b):  
         return a | b
```

```
In [51]: def nor(a, b):  
         return not a | b
```

## 0.2 Problem 3

```
In [52]: inputs = [(0, 0, 0),  
                   (0, 0, 1),  
                   (0, 1, 0),  
                   (0, 1, 1),  
                   (1, 0, 0),  
                   (1, 0, 1),  
                   (1, 1, 0),  
                   (1, 1, 1)]
```

```
In [53]: for a, b, c in inputs:  
         print((a & b) | (b & c) | (a & c))
```

```
0  
0  
0  
1  
0  
1  
1  
1  
1
```

### 0.3 Problem 4

```
In [54]: inputs = [(0, 0),
                  (1, 0),
                  (0, 1),
                  (1, 1)]
```

```
In [55]: for a, b in inputs:
          print( not ((a & b) | ((not a) & (not b))) )
```

```
False
True
True
False
```

### 0.4 Problem 5

```
In [56]: def circuit(s, i3, i2, i1, i0):
          o3 = _and(not s, i2)
          o2 = _or(_and(s, i3), _and(not s, i1))
          o1 = _or(_and(i2, s), _and(not s, i0))
          o0 = _and(i1, s)

          return o3, o2, o1, o0
```

```
In [57]: circuit(1, 1, 0, 1, 1)
```

```
Out[57]: (0, 1, 0, 1)
```

### 0.5 Problem 6

```
In [58]: inputs = [(0, 0),
                  (1, 0),
                  (0, 1),
                  (1, 1)]
```

```
In [59]: for a, b in inputs:
          print(nand(nand(a, nand(a, b)), nand(b, nand(a, b))))
```

```
False
True
True
False
```

### 0.6 Problem 7

```
In [38]: def circuit(a, b):
          return _or(_and(not a, b), _and(not b, a))
```

```
In [39]: for a, b in inputs:
          for c in [0, 1]:
            print(circuit(circuit(a, b), c))
```

```
0
1
1
0
1
0
0
1
```

## 0.7 Problem 8

```
In [45]: inputs = [(0, 0, 0),
                   (0, 0, 1),
                   (0, 1, 0),
                   (0, 1, 1),
                   (1, 0, 0),
                   (1, 0, 1),
                   (1, 1, 0),
                   (1, 1, 1)]
```

```
In [47]: for a, b, c in inputs:
          print(_or(_and(not b, not c), _and(b, c)))
```

```
1
0
0
1
1
0
0
1
```