

Problem Set 3

Justin Ely

605.411 Foundations of Computer Architecture

20 September, 2016

1)

For this, and following solutions, (n) represents column n in the table. This is used to reduce errors in typing when doing arithmetic with derived columns.

1	2	3	4	5	6	7
a	b	$(ab)'$	$A'(3)$	$B'(3)$	$((4)(5))'$	$((6)(6))'$
0	0	1	1	1	0	1
1	0	1	0	1	1	0
0	1	1	1	0	1	0
1	1	0	1	1	0	1

The result (column 7) has the same truth table as a XNOR gate.

2)

ROW	A	B	C	Y	Maxterm	Minterm
0	0	0	0	1		$A'B'C'$
1	0	0	1	0	$A + B + C'$	
2	0	1	0	1		$A'BC'$
3	0	1	1	1		$A'BC$
4	1	0	0	0	$A' + B + C$	
5	1	0	1	0	$A' + B + C'$	
6	1	1	0	1		ABC'
7	1	1	1	0	$A' + B' + C'$	

3a)

1	2	3	4	5	6	7
a	b	c	ab	bc	ac	(4) + (5) + (6)
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	0	0
1	0	1	0	0	1	1
1	1	0	1	0	0	1
1	1	1	1	1	1	1

3b)

$AB + BC + AC$

4)

1	2	3	4	5	6
a	b	ab	a'b'	(3) + (4)	(5)'
0	0	0	1	1	0
1	0	0	0	0	1
0	1	0	0	0	1
1	1	1	0	1	0

This logic circuit can be replaced with a single XOR gate.

5)

From the circuit diagram shown:

$$1. o_3 = S'I_2$$

$$2. o_2 = SI_3 + S'I_1$$

$$3. o_1 = I_2S + S'I_0$$


$$4. o_0 = I_1S$$

Thus, by setting $S = 1$, and $I_3, I_2, I_1, I_0 = 1011$, the circuit comes out as:
 $o_3, o_2, o_1, o_0 = 0101$.

6)

From problem 1, column 6 is the same output as an XOR gate, and has been constructed with only NAND gates. Thus, the circuit would look like that shown in the figure below.

Figure 1: Circuit diagram for an XOR gate using only NAND gates.

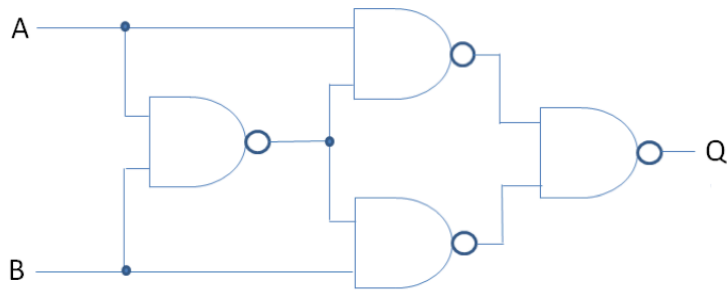

7)

1	2	3	4	5	6	7	8	9
A	B	$A'B$	AB'	$A'B + AB'$	C	$(5)'C$	$C'(5)$	R
0	0	0	0	0	0	0	0	0
0	0	0	0	0	1	1	0	1
0	1	1	0	1	0	0	1	1
0	1	1	0	1	1	0	0	0
1	0	0	1	1	0	0	1	1
1	0	0	1	1	1	0	0	0
1	1	0	0	0	0	0	0	0
1	1	0	0	0	1	1	0	1

8a)

A	B	C	Z	Minterm
0	0	0	1	$A'B'C'$
0	0	1	0	$A'B'C$
0	1	0	0	$A'BC'$
0	1	1	1	$A'BC$
1	0	0	1	$AB'C'$
1	0	1	0	$AB'C$
1	1	0	0	ABC'
1	1	1	1	ABC

The function Z is then built of the minterms on rows where Z=1: $Z = A'B'C' + A'BC + AB'C' + ABC$.

8b)

$$Z = A'B'C' + A'BC + AB'C' + ABC \quad (1)$$

$$Z = B'C'(A' + A) + BC(A' + A) \quad (2)$$

$$Z = B'C' + BC \quad (3)$$